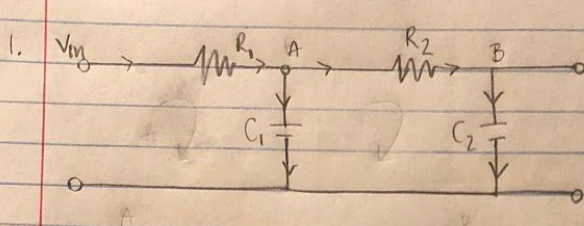


Homework 2



KCL @ node A

$$\frac{V_{in} - V_A}{R_1} = C_1 \frac{dV_A}{dt} + \frac{V_A - V_{out}}{R_2}$$

KCL @ node B

$$\left(\frac{V_A - V_{out}}{R_2} = C_2 \frac{d(V_{out})}{dt} \right) R_2 \Rightarrow V_A - V_{out} = C_2 (\dot{V}_{out}) R_2$$


$$V_A = V_{out} + C_2 R_2 \dot{V}_{out}$$

$$u = V_{in} \quad y = V_{out}$$

$$\frac{V_{in} - V_{out} + C_2 R_2 \dot{V}_{out}}{R_1} = C_1 \frac{d(V_{out} + C_2 R_2 \dot{V}_{out})}{dt} + \frac{V_{out} + C_2 R_2 \dot{V}_{out} - V_{out}}{R_2}$$

$$u - y - C_2 R_2 \ddot{y} = (C_1 (R_2 C_2 \ddot{y} + \dot{y}) + (R_2 C_2 \dot{y} + y - y)) R_1$$
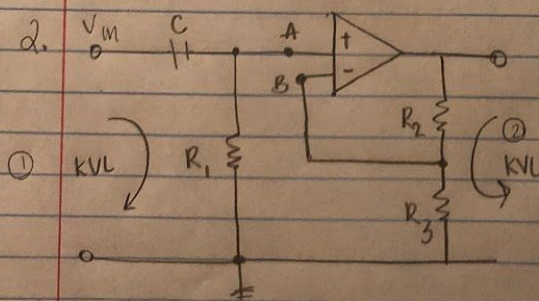
$$u = C_1 R_2 C_2 \ddot{y} + R_1 \dot{y} + R_1 C_2 \dot{y} + C_2 R_2 \dot{y} + y$$



$$V_A = e_i - \frac{1}{C} \int i_i dt \quad i = V_A / R_1$$

$$V_B = e_o \cdot \frac{R_3}{R_2 + R_3}$$

$$e_i = V_A + V_{R_1}$$


$$e_i = \frac{1}{C} \int i_i dt + R_1 i_i$$

$$e_i = \frac{1}{CR_1} \int V_A dt + V_A$$

$$e_i = \frac{1}{CR_1} \cdot \frac{R_3}{R_2 + R_3} \int e_o dt + e_o \cdot \frac{R_3}{R_2 + R_3}$$

$$\dot{e}_i = \frac{1}{CR_1} \cdot \frac{R_3}{R_2 + R_3} e_o + \dot{e}_o \cdot \frac{R_3}{R_2 + R_3}$$

3.

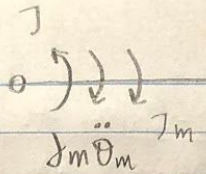

$J\ddot{\theta} \Rightarrow$ moment of inertia

$$J_m \ddot{\theta}_m = J_m - J$$

$$J_L + J_L \ddot{\theta} = 0$$

$$\text{gear ratio} = n = \frac{J}{J_L} = \frac{\theta}{\theta_m} \Rightarrow \frac{J}{J_L} = \frac{\theta}{\theta_m} \Rightarrow J = \frac{\theta}{\theta_m} J_L$$

$$J_m = J \ddot{\theta}_m + J$$

$$J_m = k_{Ti}$$

$$J = J \ddot{\theta}_m + k_{Ti}$$

$$J_m \ddot{\theta}_m = J_m - k_{Ti}$$

$$k_{Ti} = J_m \ddot{\theta}_m + \frac{\theta}{\theta_m} J_L$$

$$\left\{ \begin{array}{l} \frac{J}{J_L} = \frac{\theta}{\theta_m} \Rightarrow J = \frac{\theta}{\theta_m} (J_L) \\ \theta_m = \frac{n}{\theta} \Rightarrow \frac{\theta}{\theta_m} = n \end{array} \right.$$

$$\frac{\theta}{\theta_m} = n \Rightarrow \theta_m = \frac{\theta}{n}$$

$$J_L = J_L \ddot{\theta}$$

$$J_m = J + J_n \ddot{\theta}$$

$$k_{Ti} = J + J_n \ddot{\theta}$$



$$k_{Ti} = \frac{\theta}{\theta_m} J_L + J_m \ddot{\theta}$$

$$k_{Ti} = \frac{\theta}{\frac{\theta}{n}} J_L + J_m \frac{\theta}{n}$$

$$k_{Ti} = n \cdot J_L \ddot{\theta} + J_m \frac{\theta}{n}$$



4.

a)

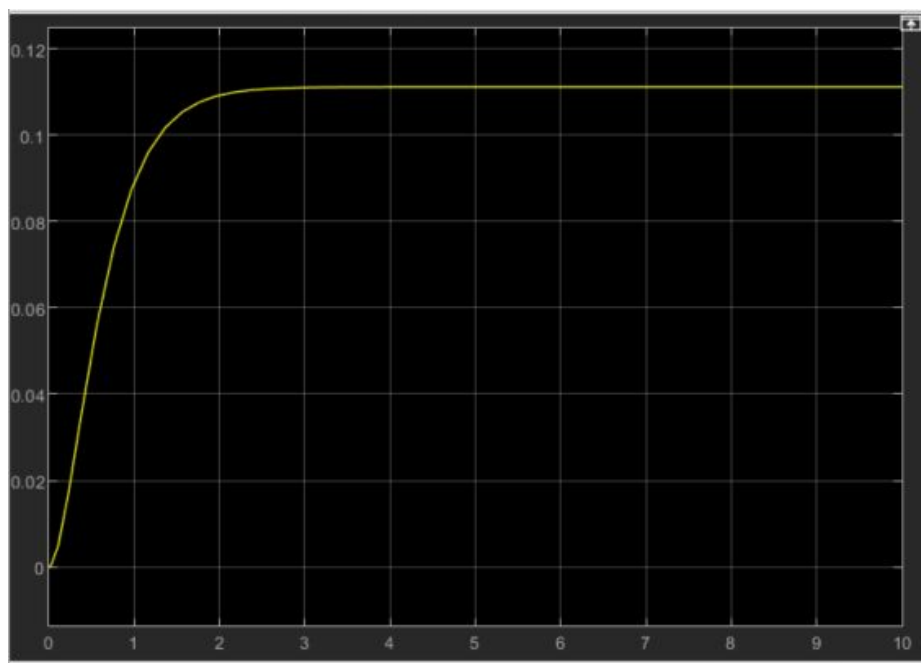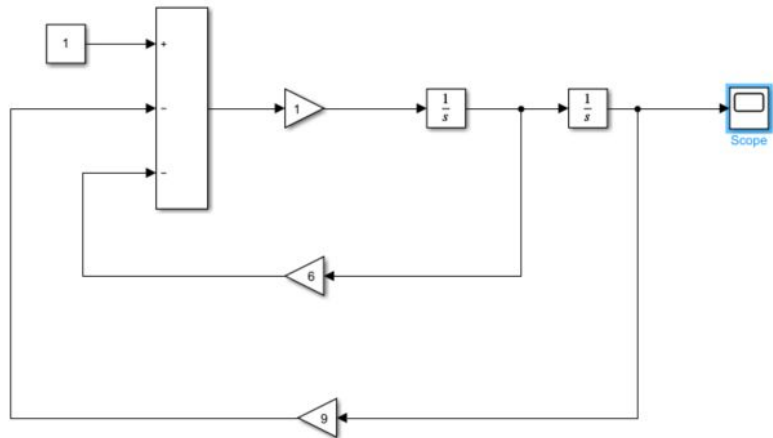



4.

b) (i)

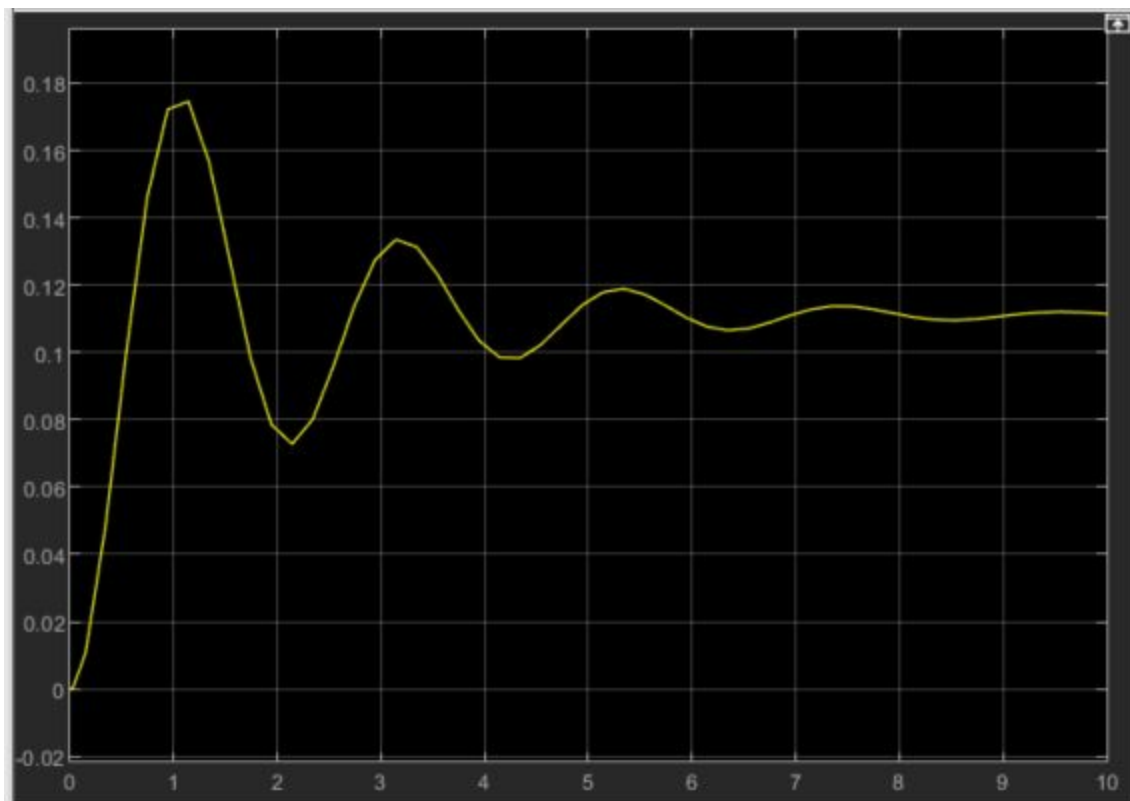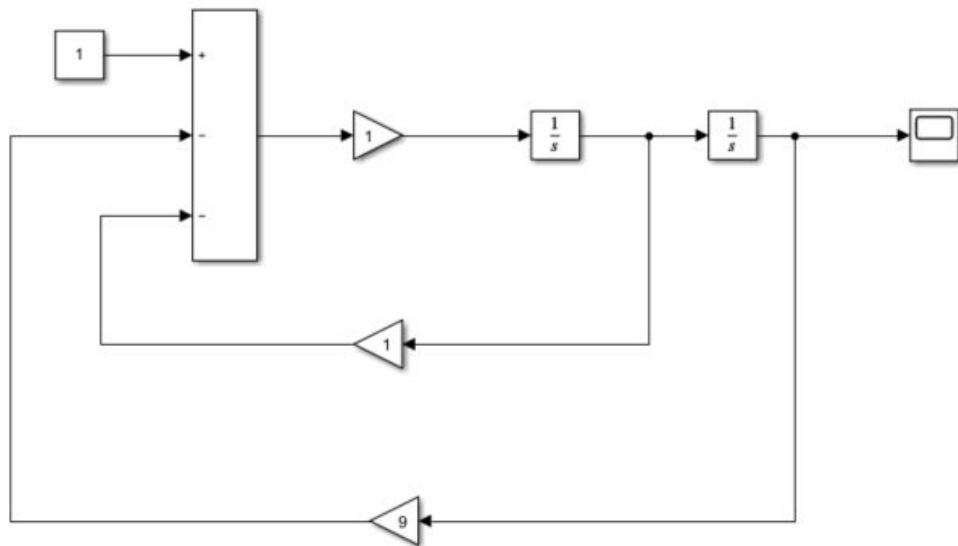

4.

b) (ii)

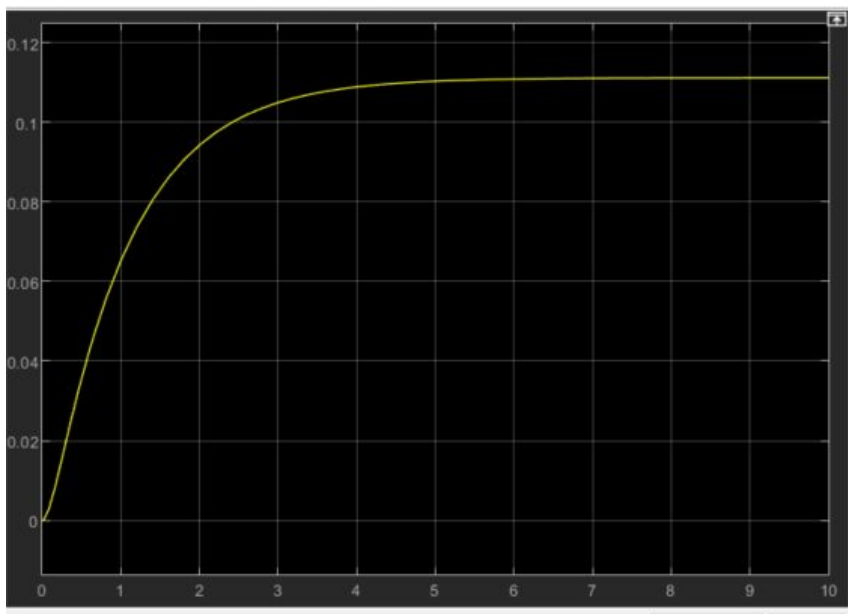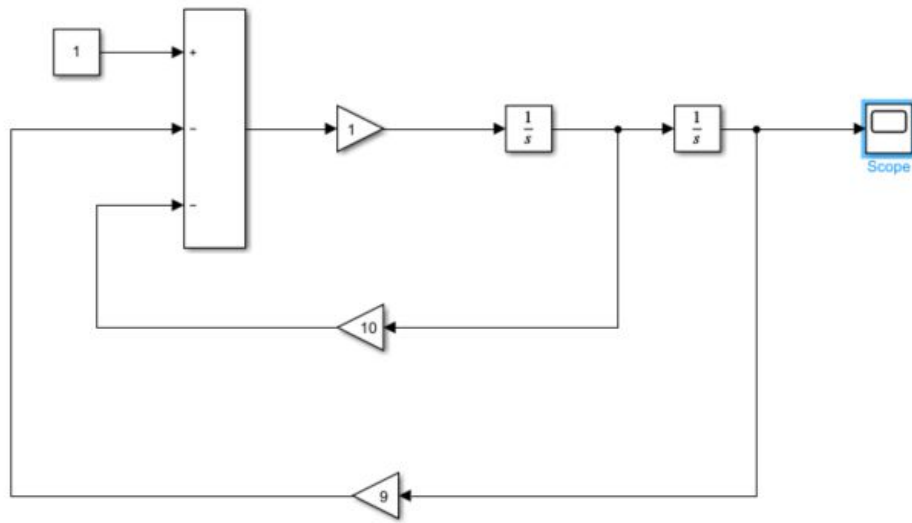

As the c-value increases, the graph steadies/levels out. The slope increases exponentially and then steadies out. There is less deviation and the y-values stay about the same as the time increases.