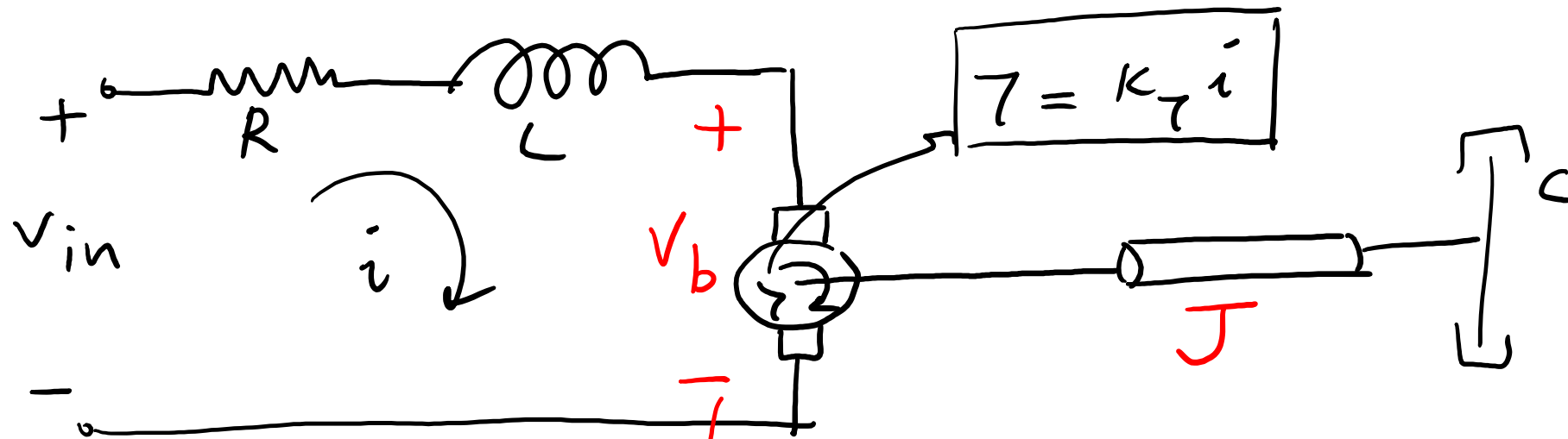


Dynamics of a DC Motor:

↳ Apply a voltage \rightarrow rotational motion



"load" voltage due to the rotation
of the armature (AKA Back EMF)

$$V_b = K_b \frac{d\theta}{dt}$$

Elec: (KVL)

$$v_{in} = R\bar{i} + L \frac{d\bar{i}}{dt} + v_b$$

Mech: (Newton's 2nd law)

$$J\ddot{\theta} = \tau - c\dot{\theta}$$

$k_b \dot{\theta}$

$k_T i$

$$k_T i = J\ddot{\theta} + c\dot{\theta}$$

$$\bar{i} = \frac{J}{k_T} \ddot{\theta} + \frac{c}{k_T} \dot{\theta}$$

$$v_{in} = \underbrace{\frac{RJ}{k_T} \ddot{\theta} + \frac{RC}{k_T} \dot{\theta}}_{k_i} + \underbrace{\left(\frac{LJ}{k_T} \right)^{(3)} \ddot{\theta} + \frac{LC}{k_T} \dot{\theta}}_{L \frac{d\bar{i}}{dt}} + \underline{k_b \dot{\theta}}$$

$$\omega = \dot{\theta}$$


$$\boxed{V_{in}} = \cancel{\frac{LJ}{k_z} \ddot{\omega}} + \cancel{\left(\frac{LC + RJ}{k_z} \right) \dot{\omega}} + \left| \left(\frac{RC}{k_z} + k_b \right) \omega \right|$$

For small L :

$$\left[V_{in} = \frac{RJ}{k_z} \ddot{\theta} + \left(\frac{RC}{k_z} + k_b \right) \dot{\theta} \right] \frac{k_z}{R}$$

$$J \ddot{\theta} + \left(c + \frac{k_b k_z}{R} \right) \dot{\theta} = k_z \frac{V_{in}}{R}$$

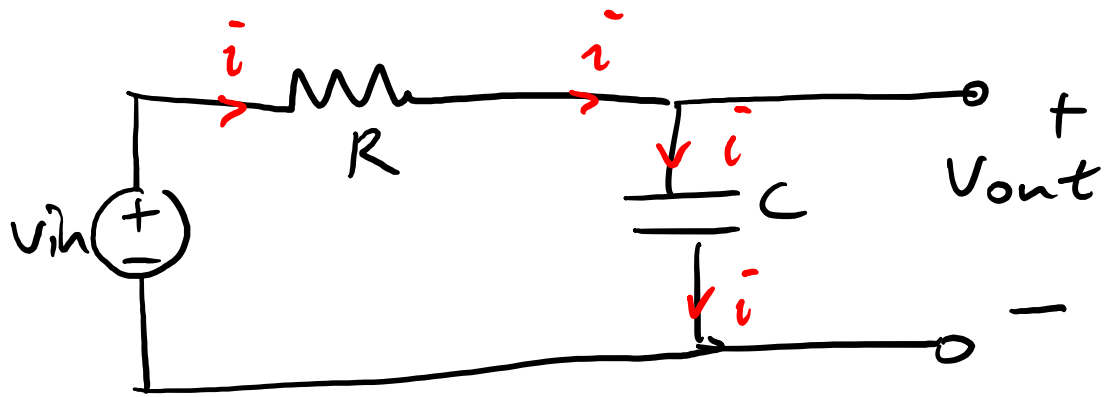Back EMF acts as viscous friction!
damping



$$\underline{V_{in}} = \overset{\substack{\uparrow \\ i = C \frac{dV_{out}}{dt}}}{iR} + V_{out}$$

$$\boxed{V_{in} = RC \dot{V}_{out} + V_{out}}$$

Natural (free) Response:

$$v_{in} = 0$$


$$(RC) \dot{V}_{out} + V_{out} = 0 \quad (\text{1st order ODE})$$

$$V_{out} = k e^{-t/RC}$$

$$\uparrow$$

$$V_0 = V_{out}(0)$$
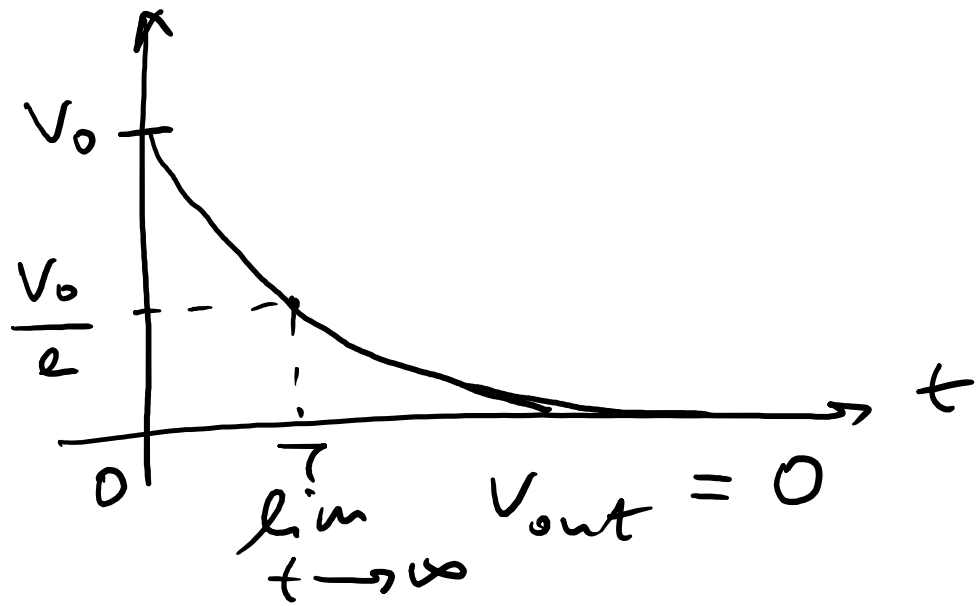
$$\Rightarrow \boxed{V_{out} = V_0 e^{-t/RC}}$$



Forced Response

$V_{in} = \text{constant}$

$$\frac{V_o}{e} = V_o e^{-\tau/RC} \Rightarrow \boxed{\tau = RC}$$

$\tau = RC$: time constant

the time required for the voltage to fall to V_o/e .

$$RC \dot{V}_{out} + V_{out} = V_{in} \equiv \text{constant}$$

$$V_{out} = K_1 e^{-K_2 t} + K_3$$

free response
(transient)

forced response
(steady-state)

$$V_{out} = -K_1 K_2 e^{-K_2 t}$$

$$RC \underbrace{(-K_1 K_2 e^{-K_2 t})}_{V_{out}} + \underbrace{K_1 e^{-K_2 t} + K_3}_{V_{out}} = V_{in}$$

$$K_3 = V_{in}$$

$$RC \underbrace{(-K_1 K_2 e^{-K_2 t})}_{V_{out}} + \underbrace{K_1 e^{-K_2 t}}_{V_{out}} = 0$$

$$(K_1)(e^{-K_2 t})(1 - RC K_2) = 0$$

$$\cancel{K_1 = 0}$$

$$\cancel{e^{-K_2 t} = 0}$$

$$1 - RC K_2 = 0 \Rightarrow K_2 = \frac{1}{RC} = \frac{1}{\tau}$$

$K_1 = ?$ use initial value

$$V_{out}(0) = V_0$$

$$V_{out} = K_1 e^{-t/RC} + V_{in}$$

$$V_{out}(0) = K_1 + V_{in} = V_0$$

$$K_1 = V_0 - V_{in}$$

Vout



When $v_R = 0$

$$\Rightarrow \underline{V_{out}(t) = V_0 e^{-t/RC}}$$

time constant: $\tau = RC$

$$\lim_{t \rightarrow \infty} V_{out} = V_{in}$$

transient

Steady-state


* We have 2 significant problems:

1) we don't know how to use diff. eqn's as system models in block diagrams.

2) It is very difficult to solve these eqn's in time domain for CENTRAL input func'.

Solution:


LAPLACE TRANSFORM

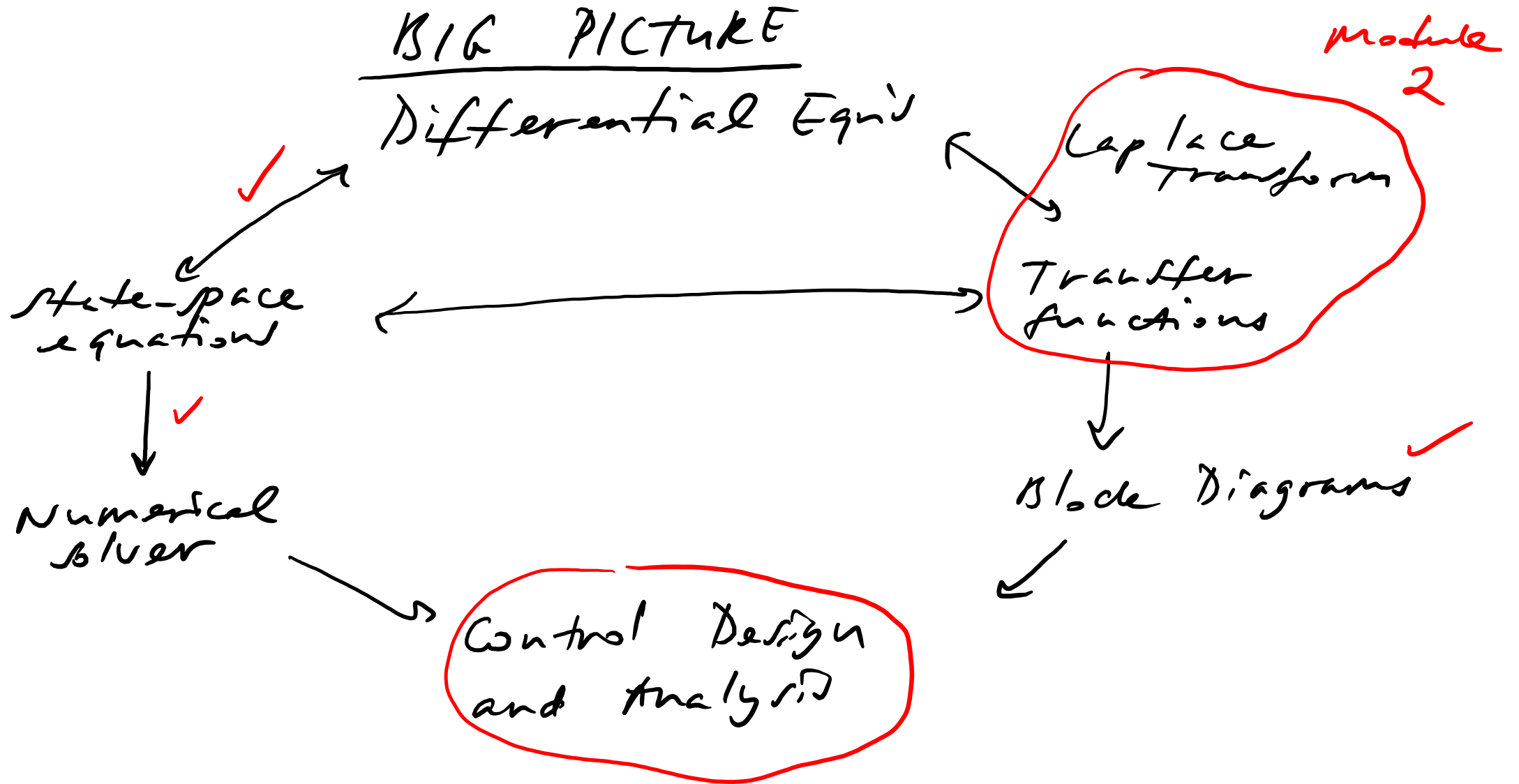

Standard Input Functions

Unit Step Function:

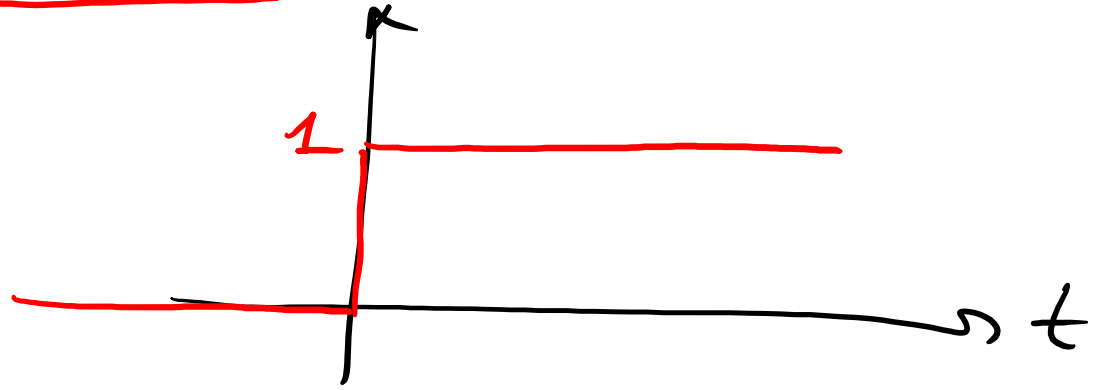
$$\textcircled{u(t)} = \underline{1(t)} = \begin{cases} 1, & t \geq 0 \\ 0 & \text{otherwise} \end{cases}$$



$V_{in. 1(t)} \rightarrow$ A step input of V_{in} at $t=0$.

Unit Ramp Function:
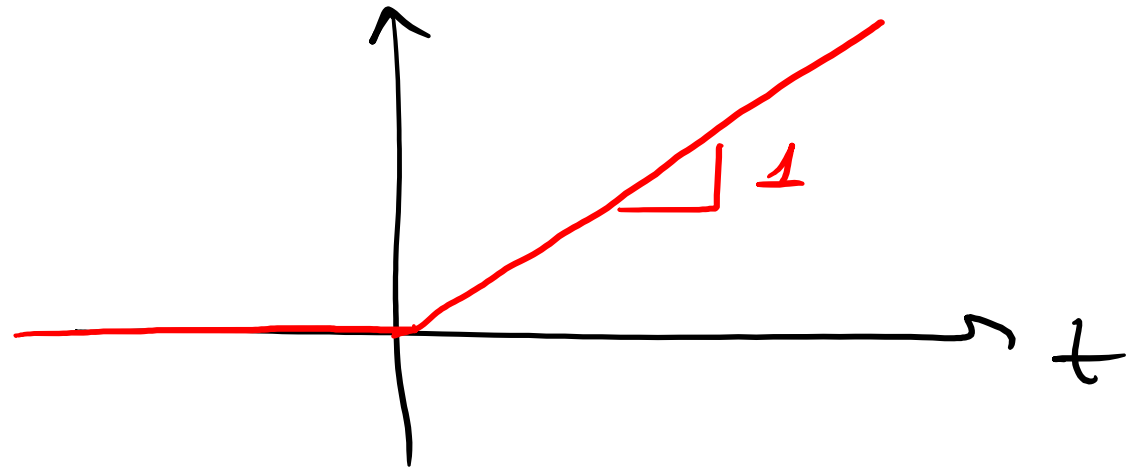
$$r(t) = \begin{cases} t, & t \geq 0 \\ 0 & \text{otherwise} \end{cases}$$



Unit Impulse Function (Dirac Delta)

Defined only $t=0$

$$\delta(t) = 0 \quad t \neq 0$$

$$\int_{-\infty}^{\infty} \delta(t) dt = 1$$

